

## GENERAL EXERCISES

- 6.1 Explain why two registers are needed rather than a single edge-triggered register to make a DAC function with a  $\mu\text{P}$  and also in flow-through mode.
- 6.2 The binary-weighted DAC of Fig. 6-4 has a maximum output voltage of +10 V. If  $R_F = 40 \text{ k}\Omega$  and  $V_B = -4 \text{ V}$ , select values of  $R_3$ ,  $R_2$ ,  $R_1$ , and  $R_0$  to achieve the maximum possible conversion factor.
- 6.3 Repeat problem 6.2 for a 6-bit DAC. In this case, find values of  $R_5$ ,  $R_4$ ,  $R_3$ ,  $R_2$ ,  $R_1$ , and  $R_0$ . What is the  $CF$  in this circuit?
  
- 6.4 In Fig. 6-5, assume that  $R_F = 4 \text{ k}\Omega$ ,  $R_0 = 20 \text{ k}\Omega$ , and  $V_{REF} = 8 \text{ V}$ . What is  $V_A$  for an input code of 1010?
- 6.5 In problem 6.4, select  $R_F$  to create a conversion factor of 0.6 V.
- 6.6 The LSB resistor in a 6-bit binary-weighted DAC is  $320 \text{ k}\Omega$ . What is the value of the MSB resistor? What is the change in absolute value of MSB resistance to cause a worst-case change in  $V_A$  of  $\pm 1/2$  LSB?
- 6.7 The ladder DAC of Fig. 6-6(a) has  $R_F = 20 \text{ k}\Omega$ ,  $V_{REF} = -12 \text{ V}$ , and is an 8-bit DAC. Calculate  $R$  to result in  $CF = 0.04 \text{ V}$ . Calculate the output voltage for an input code of 10011101.
- 6.8 If the conversion factor of an 8-bit ladder DAC is  $0.04 \text{ V}$  and  $V_{REF} = -12 \text{ V}$ , calculate the change in  $V_{REF}$  to cause a  $\pm 1/2$  LSB change in  $V_A$ .
- 6.9 If  $R_F = 20 \text{ k}\Omega$  and  $R = 20 \text{ k}\Omega$ , select  $V_{REF}$  to give a  $CF = 0.8 \text{ V}$  in the circuit of Fig. 6-10.
- 6.10 Suppose one has an 8-bit converter and a 7-bit converter. The analog output ranges of both converters are 0–10 V. What is the LSB value of each converter? Now explain how applying 7 bits to the 8-bit converter (LSB of the 8-bit converter unused) results in the same quantum interval as the original 7-bit converter.
- 6.11 Derive Eq. (6-12) for the BCD DAC. Show that Fig. 6-8 performs the correct conversion for the code 100101010111.